

OHMS LAW

Key Revision Facts: GCSE Science

Current, Voltage, and resistance are all related using Ohm's law.

V = Volts

R = Resistance

I = Current

$$V = I \times R$$

Examples

- What resistance is needed to pass 5a with a voltage of 100v

$$R = \frac{V}{I}$$

$$R = \frac{100}{5}$$

$$R = 20\Omega$$

- What Voltage is need to allow a current of 3a through a resistance of 400Ω?

$$V = I \times R$$

$$V = 3 \times 400$$

$$V = 1200v$$

- What current passes through a 10Ω Resistor with a voltage of 60v?

$$I = \frac{V}{R}$$

$$I = \frac{60}{10}$$

$$I = 6a$$